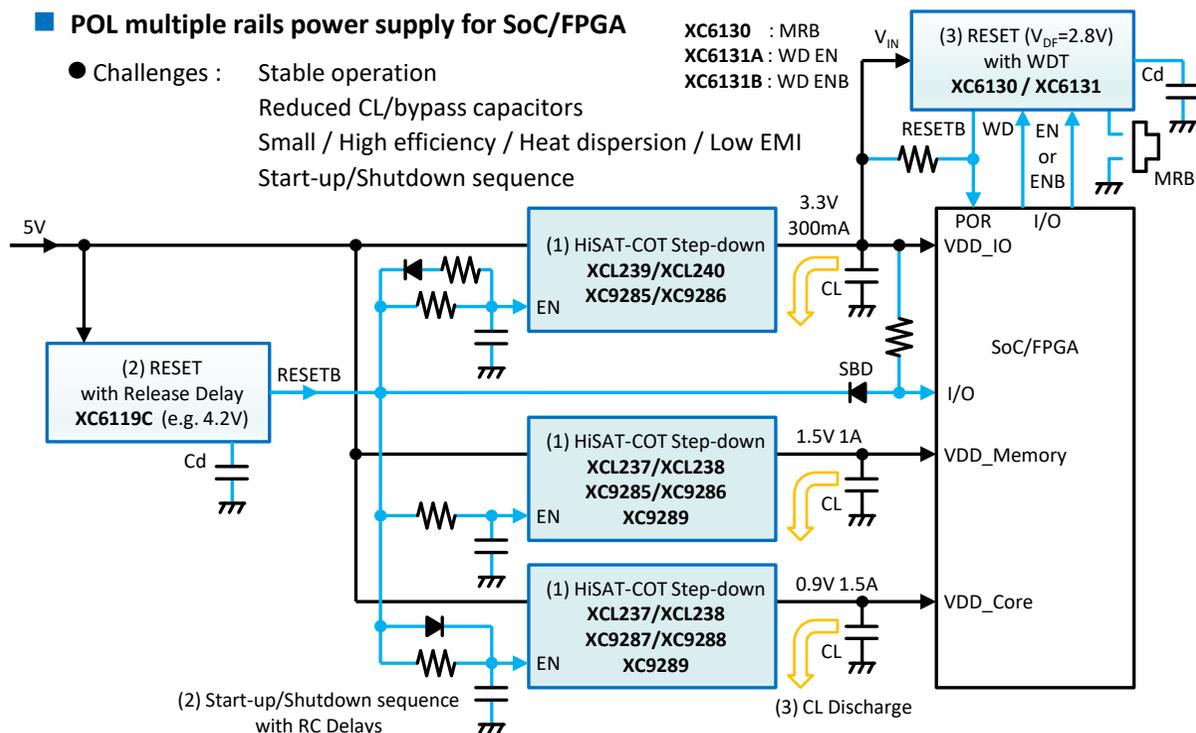



# 5V : POL Solutions for Multiple Power Rails

## ■ POL multiple rails power supply for SoC/FPGA

- Challenges : Stable operation
- Reduced CL/bypass capacitors
- Small / High efficiency / Heat dispersion / Low EMI
- Start-up/Shutdown sequence



## (2) Start-up/Shutdown power sequence

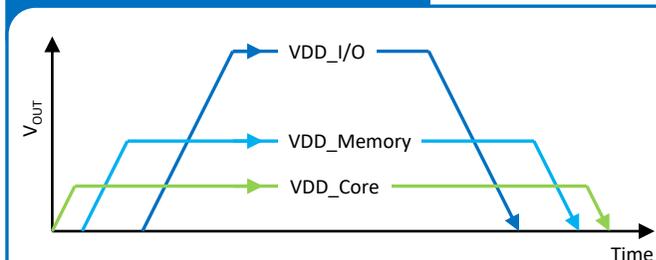

Sequence control of both rising and falling is realized with Reset IC XC6119C and RC delay to EN of each DC/DC. The CL discharge function is used for the falling.

- The delay for each DC/DC to start turning ON/OFF is,
 
$$t_{\text{delay(ON)}} = R \times C \times (-\ln((V_{\text{IN}} - V_{\text{EN}}) / V_{\text{IN}}))$$

$$t_{\text{delay(OFF)}} = R \times C \times (-\ln(V_{\text{EN}} / V_{\text{IN}}))$$
 \*  $V_{\text{EN}}$  is the threshold voltage of EN
- Set RC delays considering the soft-start time of each DC/DC and the discharge time by CL discharge.

Block	Product	Features
(1) Step-down DC/DC	<b>XCL239 / XCL240</b> <small>NEW</small>	Built-in inductor, HiSAT-COT, F-PWM, PWM/PFM 3MHz, 1A
	<b>XCL237 / XCL238</b> <small>NEW</small>	Built-in inductor, HiSAT-COT, F-PWM, PWM/PFM 3MHz, 1.5A
	<b>XC9285 / XC9286</b> <small>NEW</small>	HiSAT-COT, F-PWM, PWM/PFM 1.2MHz, 1A
	<b>XC9287 / XC9288</b> <b>XC9289</b> <small>NEW</small>	HiSAT-COT, F-PWM, PWM/PFM, MODE selectable 1.2MHz/3MHz, 1.5A
(2) RESET IC	<b>XC6119</b>	Low Iq, External Cd Release Delay
(3) WDT	<b>XC6130 / XC6131</b>	WDT/Release delay adjustable by an external Cd MR (XC6130) or WD ON/OFF control (XC6131)

## (1) Step-down DC/DC for FPGA/SoC (POL converter)

High-speed transient response HiSAT-COT controlled DC/DC arranged as POL. Built-in inductor Micro DC/DC realizes miniaturization and low EMI.  
(XCL239/XCL240, XCL237/XCL238)

## (3) Freeze countermeasure with Watchdog timer : XC6130/XC6131

Monitoring of 3.3V line voltage and detection of freezing by the WD function. In case of abnormality, SoC/FPGA is automatically restarted. Manual reset function is also available (XC6130)

# HiSAT-COT® Control for Fast Transient Response

## ■ TOREX original COT control : HiSAT-COT®

### ● Technical trend and challenges


- Stable power supply including transient response to MCU/SoC/FPGA, etc.
- Miniaturization of circuits including peripheral components, and low EMI.

### ● TOREX Proposal : HiSAT-COT® controlled Step-down DC/DC converter

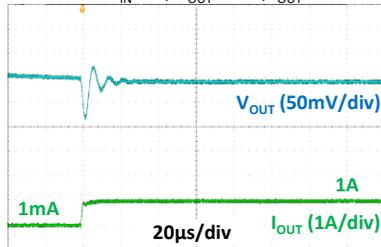
#### ➤ Significantly faster transient response

- Compared to conventional PWM and PWM/PFM control, it achieves **overwhelmingly fast response** and thus **good voltage stability**.

HiSAT-COT®  $V_{IN}=5V, V_{OUT}=1.8V, I_{OUT}=1mA \rightarrow 1A$



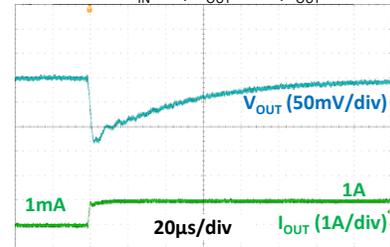Conventional  $V_{IN}=5V, V_{OUT}=1.8V, I_{OUT}=1mA \rightarrow 1A$



#### ➤ Miniaturization including peripheral components

- High-speed transient response enables **significant reduction of large capacitance** required due to lack of response of conventional PWM.
- Unlike conventional PWM phase compensation, load capacitance CL can be reduced. Also **supports a significant reduction in effective capacitance due to the bias effect of ultra-small Ceramic capacitors**.

HiSAT-COT®



Conventional




## Overview of COT control and HiSAT-COT®

### What is COT (Constant on time) control?

- PFM control with the "ton" determined by  $V_{IN}$  and  $V_{OUT}$  voltages, resulting that appears to be PWM control with constant frequency ( $f_{osc}$ ).  
**High-speed PFM comparator enables fast transient response.**
- Generate "ton" in CCM of the targeted  $f_{osc}$  from the  $V_{IN}$  and  $V_{OUT}$  set voltages so that it appears to be a constant frequency PWM control.
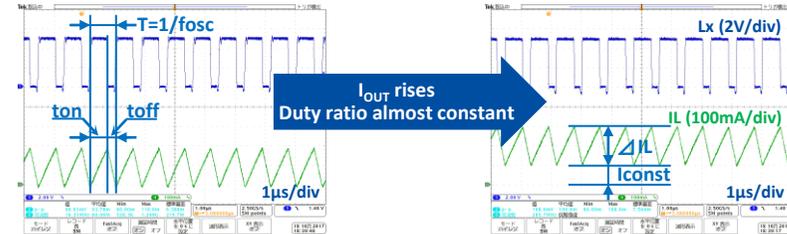
### ● CCM (Continuous Conduction Mode) operation



- Ideal Duty ratio and  $ton$  of step-down DC/DC at CCM PWM operation are  
 $ton = (1/f_{osc}) \times Duty = (1/f_{osc}) \times (V_{OUT} / V_{IN})$ .  
If there is no loss, **Duty ratio is constant** even if  $I_{OUT}$  rises.

### ● How to determine the oscillation frequency of COT control

- Generate the  $ton$  of COT control to be the  $ton$  of ideal PWM control.
- Continuous mode operation with this  $ton$  operates with the same duty as PWM control at the oscillation frequency  $f_{osc}$ .

### ● COT issues and HiSAT-COT®

HiSAT-COT improves the issues of COT control with its own circuits.

- Improved issue of increased oscillation frequency due to output current.
- Improved the deterioration of load stability with an original circuit with an additional amplifier.

# TOREX Built-In Inductor Micro DC/DC for Achieving Small / Low EMI

## TOREX original Built-in inductor Micro DC/DC XCL Series


### ● Technical trend and challenges

- For stable operation of devices, it is important to place power supply ICs close to MCUs and FPGAs. Especially in cases where multiple power supplies are required, selecting power supply ICs suitable for POL (Point of Load) is a challenge.
- Miniaturization of power circuits including ICs and low EMI are essential.

### ● TOREX Proposal : Built-in inductor Micro DC/DC
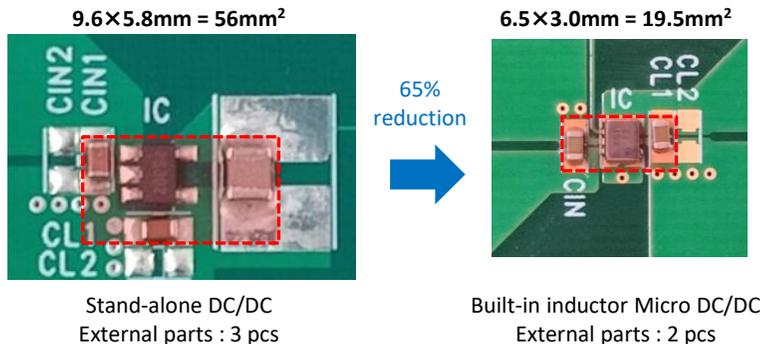
#### ➢ Significant miniaturization of power supply circuit


- Achieves a significant reduction in mounting area and providing smallest class of power supply solution.
- Unique package structure / Optimum inductor for the internal IC.
- Efficient heat dissipation performance with structures that connect IC/coil and substrate with low thermal resistance.



#### ➢ EMI reduction due to unique Built-in inductor structure

- ✓ The pocket-type structure covering the IC with a coil and the optimum placement of the IC enable a **significant reduction of radiated noise** compared to the stand-alone IC.
- ✓ Can be placed near RF ICs/Sensors, etc., contributing to miniaturization.
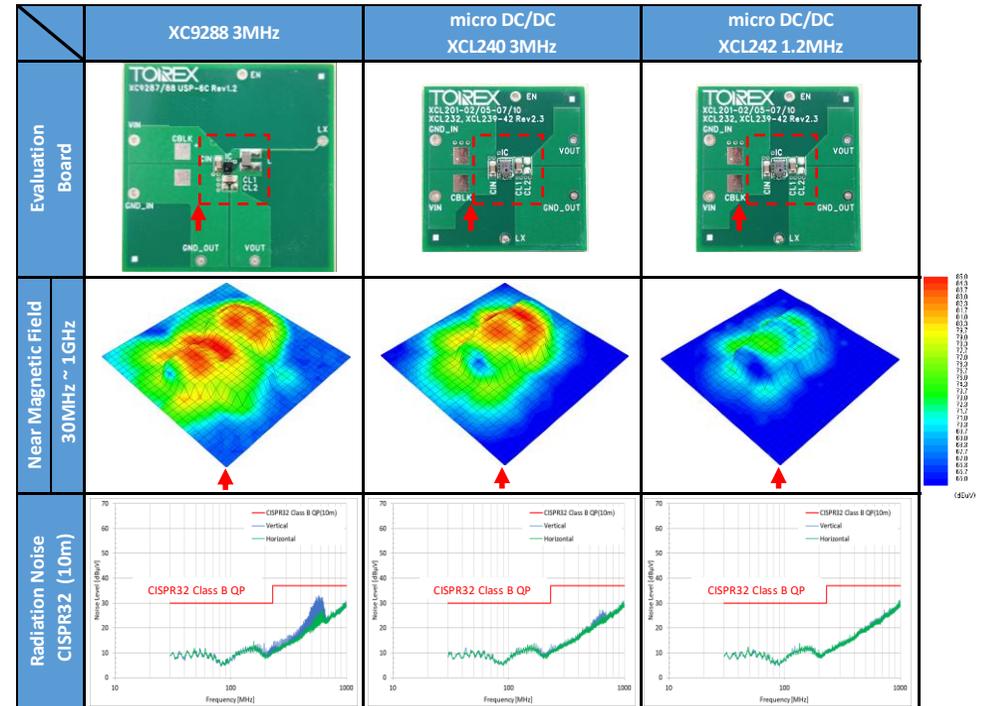
## EMI comparison of Built-in inductor Micro DC/DC and stand-alone DC/DC



### Benefits of POL (Point of Load) power supply and Micro DC/DC & HiSAT-COT®

- Shorter power supply wiring length. In addition to stable operation, reduced capacitors. Heat source dispersion facilitates heat dissipation.
- Using Micro DC/DC XCL Series with built-in inductor for POL converter enables further miniaturization, lower EMI, and easier design.
- HiSAT-COT** provides highly stable power supply, including transient response.

